

Electronics + Microcontroller

Project Name

Exercise 1: NightLight Circuit

Our Goal

To design a circuit that turns on an LED when the room becomes dark.

Necessary materials

This exercise introduce you in the electronics needed to calibrate sensors. It doesn't use the microcontroller.

The circuit uses a **bipolar transistor** (BJT) and a **differential comparator**.

MATERIAL:


- Cables.
- Potentiometer 470K.
- Bipolar junction transistor 547C.
- LED.
- LDR Sensor.
- R: 220 Ω , 100K Ω , 470K Ω .


First circuit

Night light circuit using a BJT.

Let's see the circuit schematic. Additional videos on how to assemble it are available here:


[Video](#)

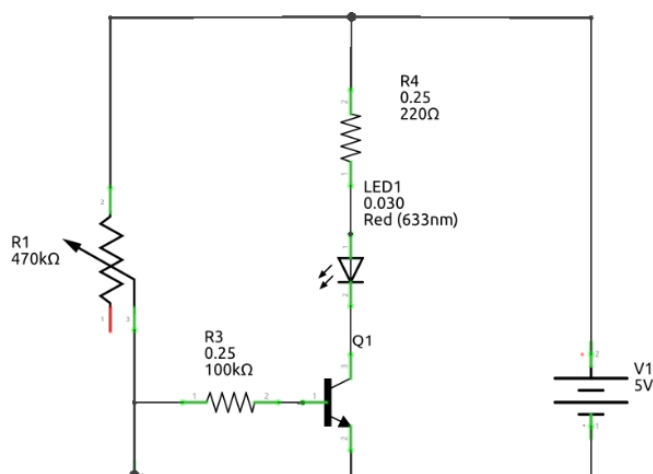

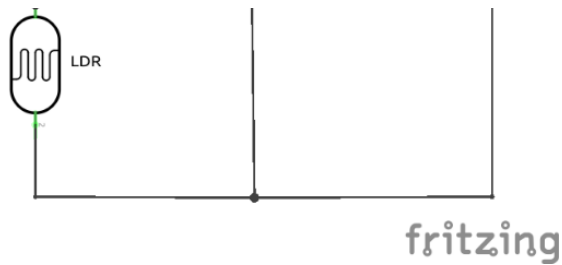

Obtained results

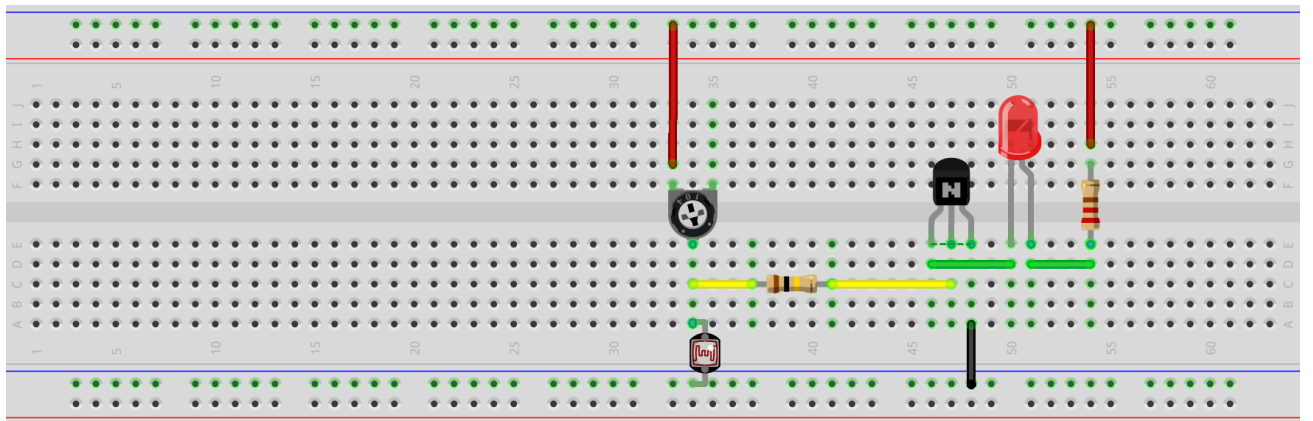HELP: This is how to wire the circuit on your protoboard:



Second circuit

Necessary materials



In this second approach, we use a **comparator instead of the bipolar transistor**. In particular, the LM393 IC that consists of two independent voltage comparators designed to operate from a single power supply over a wide range of voltages (2 to 38 V).

MATERIAL:

- Cables.
- Potentiometer 10K.
- LM393.
- LED.
- LDR Sensor.
- R: 33K Ω , 330 Ω .

Let's see the circuit schematic. Additional videos on how to assemble it are available here:


[Video](#)

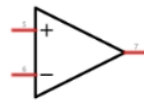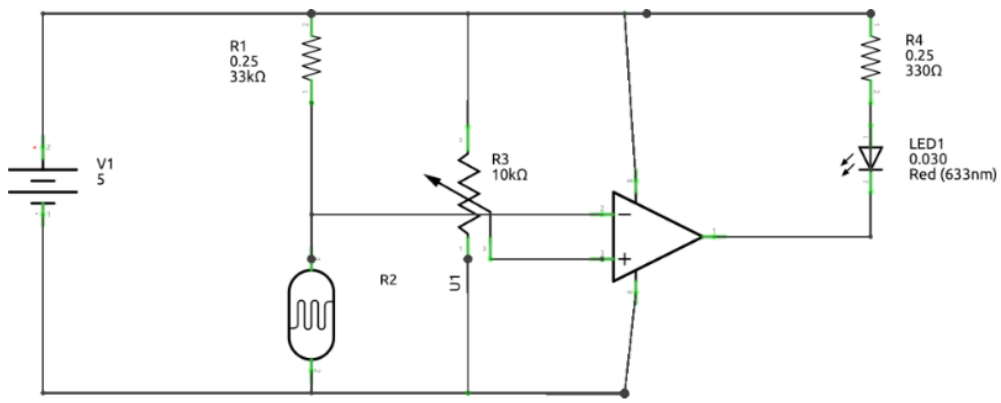


fritzing

Obtained results

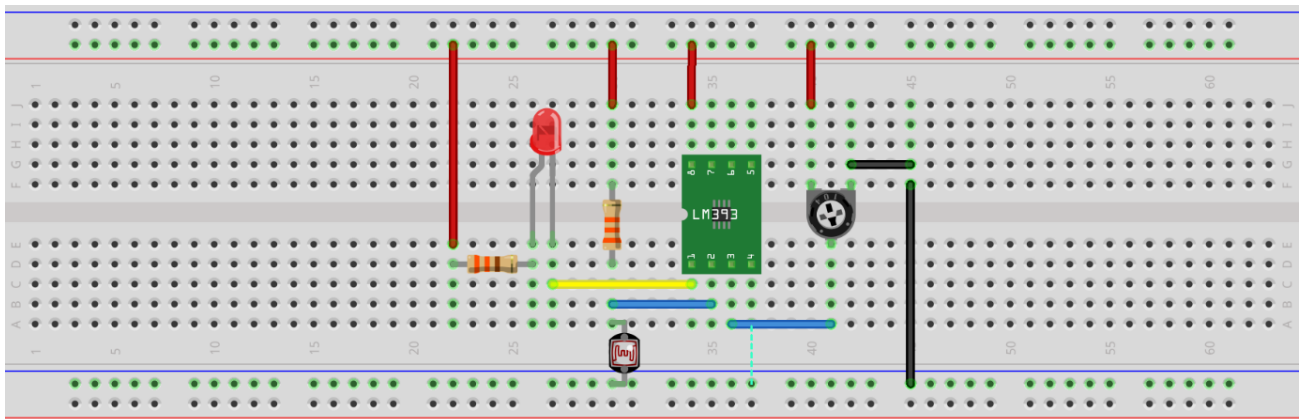HELP: This is how to wire the circuit on your protoboard:



fritzing

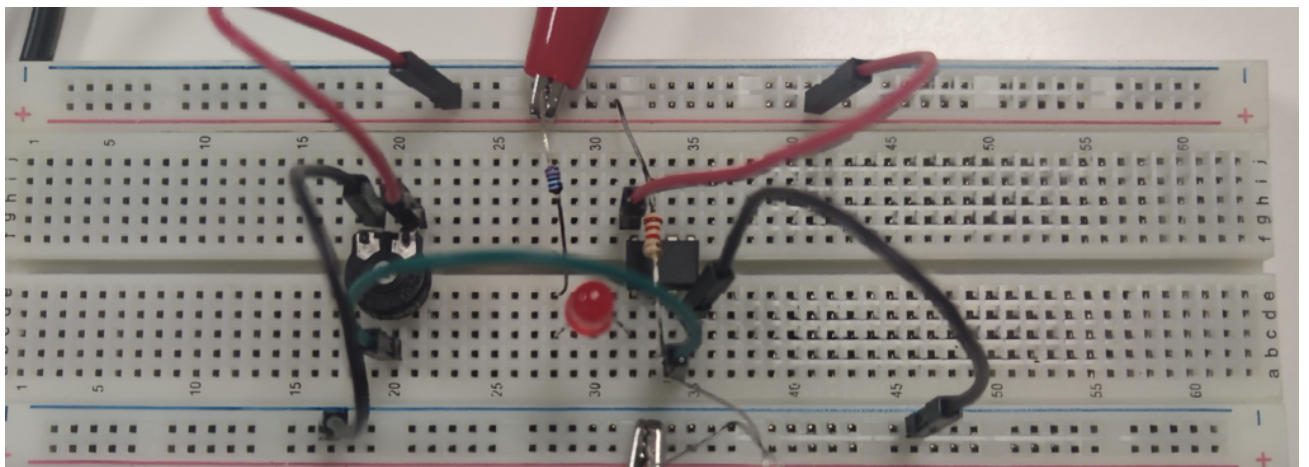

Project Name

Exercise 2: Gas control using a microcontroller

Our Goal

Activate a FAN depending on the parameters given by a gas sensor.

Third circuit

Necessary materials


We introduce the microcontroller board to manage a FAN (actuator) depending on the gas levels given.


MATERIAL:

- Cables
- Gas Sensor MQ-135
- R: 18k Ω , 620 Ω and 3,6K Ω
- BJT (Bipolar junction transistor)
- FAN
- Diode: 1N4007
- FACILINO microcontroller board (with or without multisensor shield)

Gas Sensor and Fan circuit

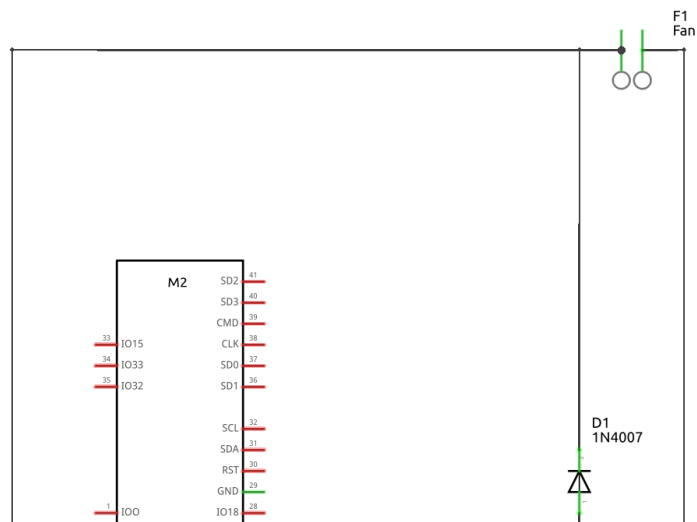
Let's see the circuit schematic. Use A3 pin to connect the Gas Sensor; and D7 to connect the FAN circuit. Additional videos on how to assemble it are available here: [Video](#)



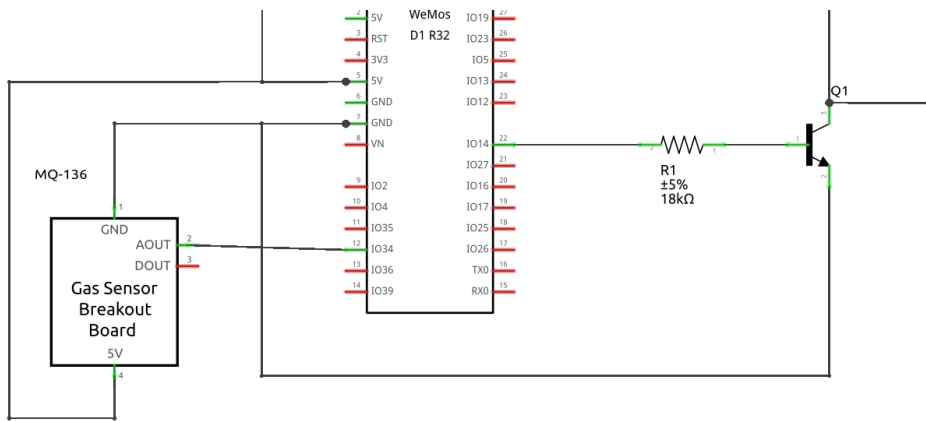

Obtained results

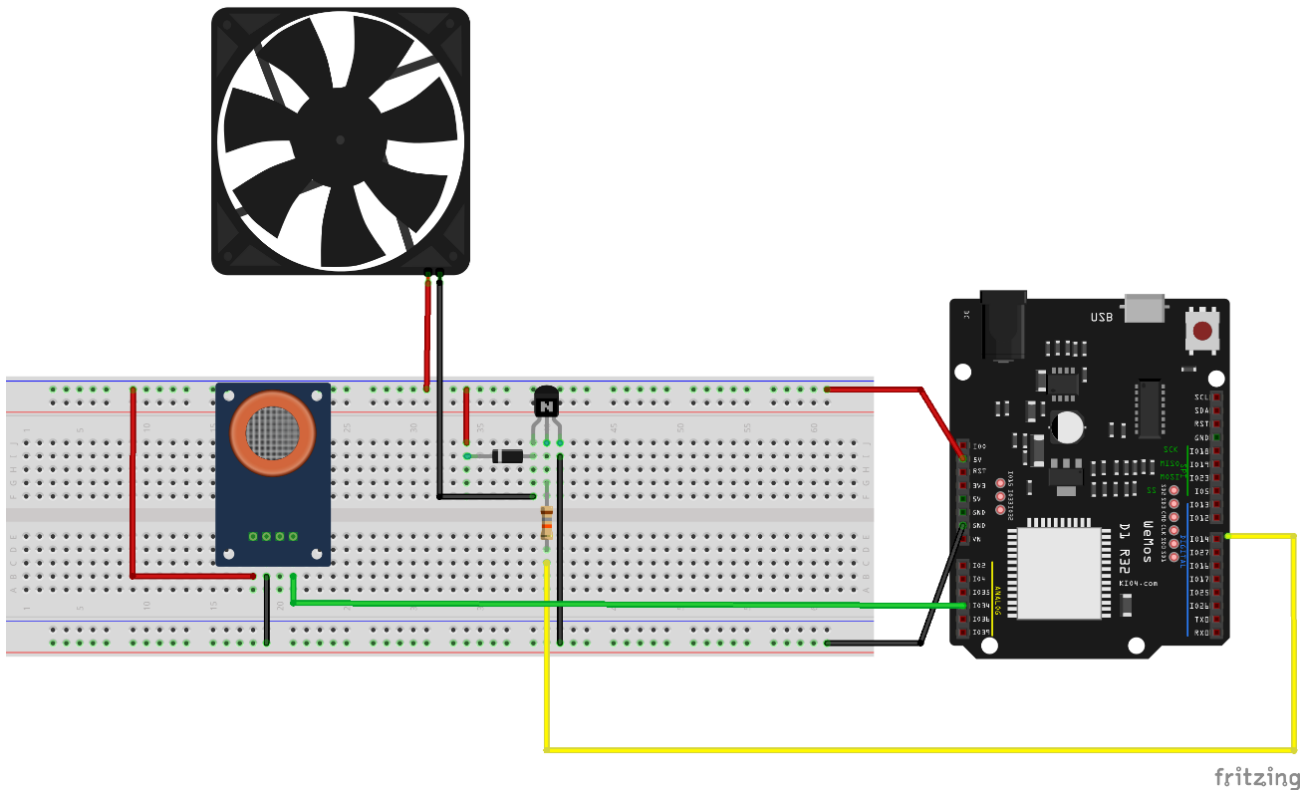HELP: This is how to wire the circuit on your protoboard:



Fourth circuit

Necessary materials



Finally, we introduce BLE (BlueTooth Low Energy) to plug a Master and Slave. Thus, we need TWO Esp32 boards (one acts as master and another acts as slave). The master will support the GAS Sensor circuit, while the slave supports the FAN circuit.




- Cables
- Gas Sensor MQ-135

- R: 18k Ω , 620 Ω and 3,6K Ω
- BJT (Bipolar junction transistor)
- FAN
- Diode: 1N4007
- FACILINO microcontroller board (with or without multisensor shield)

ESP32 BLUETOOTH circuit

Schematic and protoboard views:

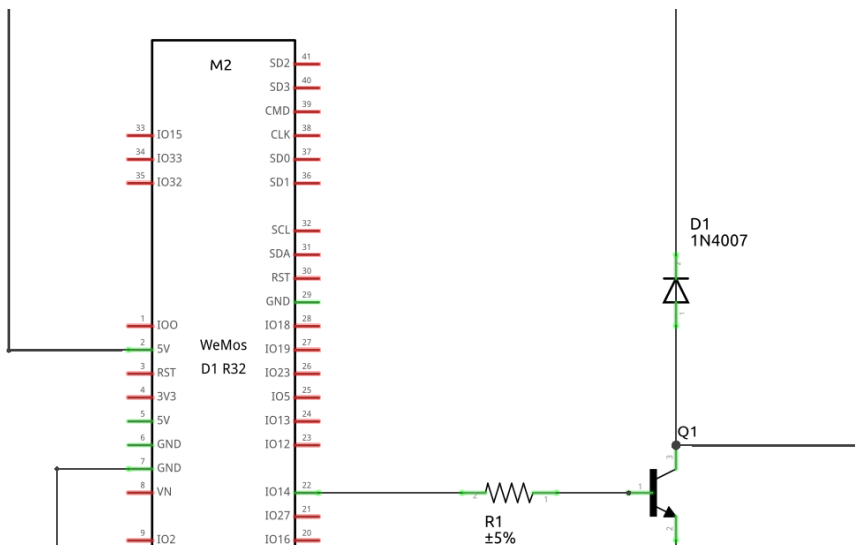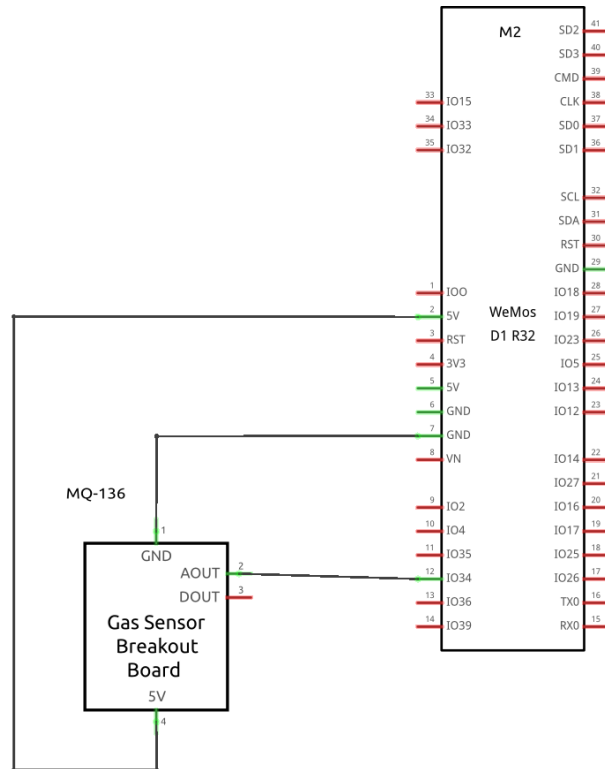

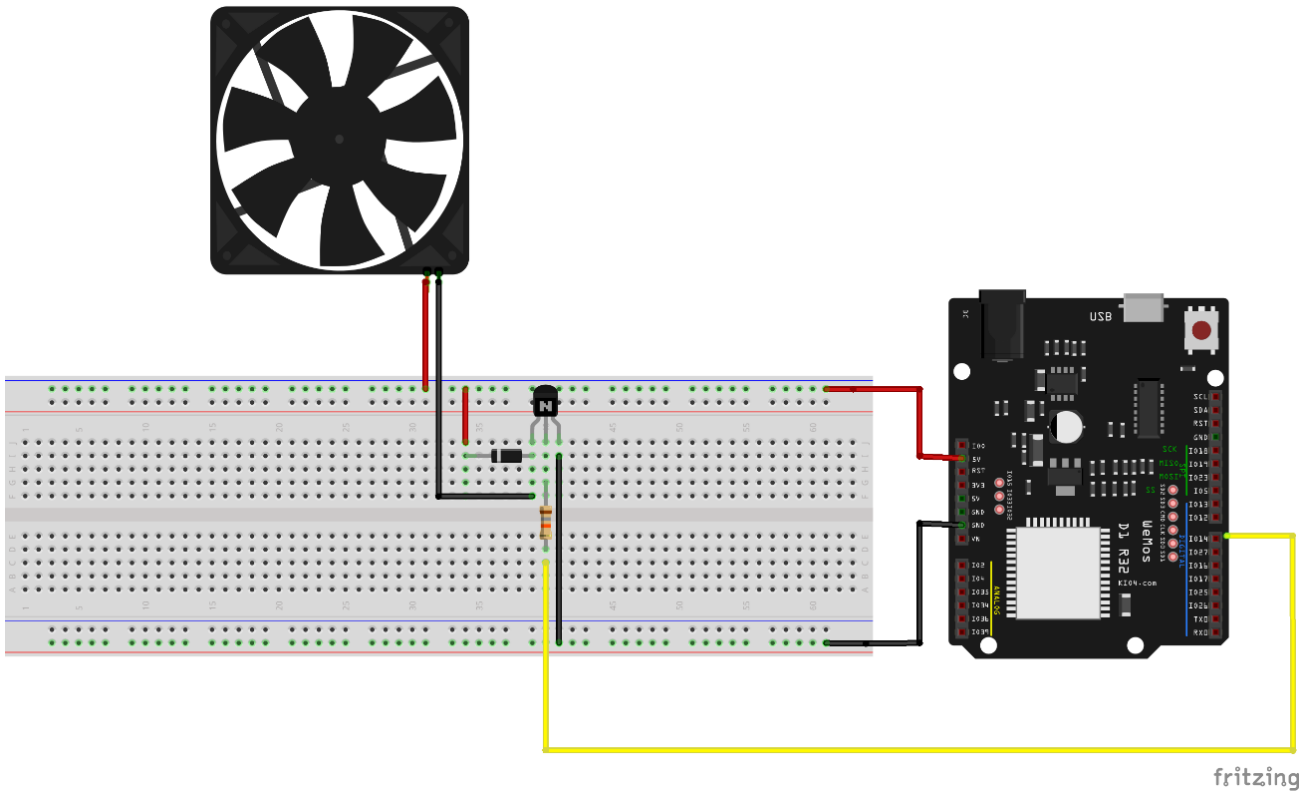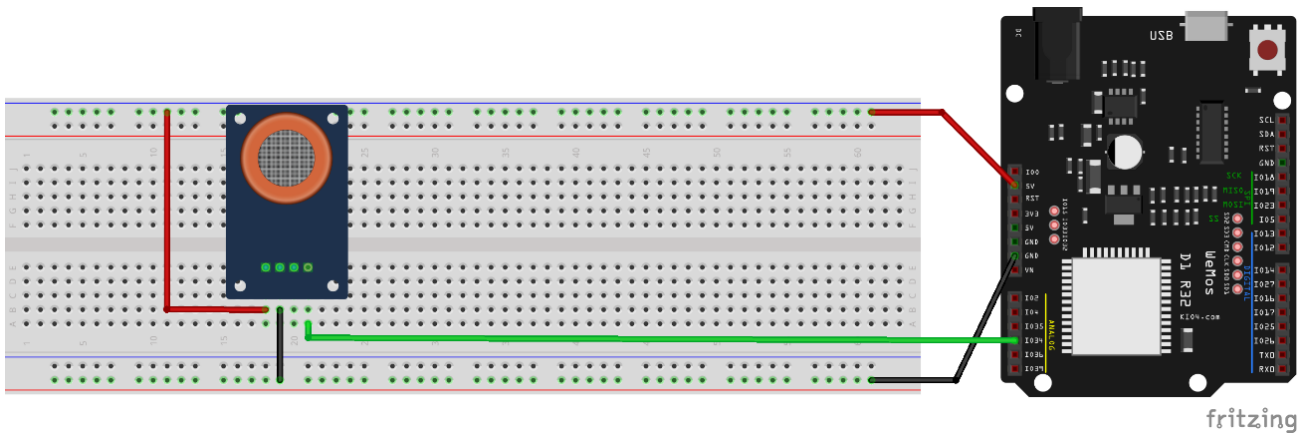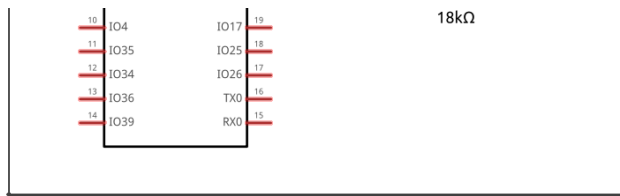

Obtained results

Here is a [video](#) of how to assemble the circuit and also the [codes](#) that must be implemented in the ESP32 boards.