




# ELSE PRO

## WEBINAR 3 – PART 1

*Using sensors and actuators for practical experiments*

José V. Benlloch-Dualde

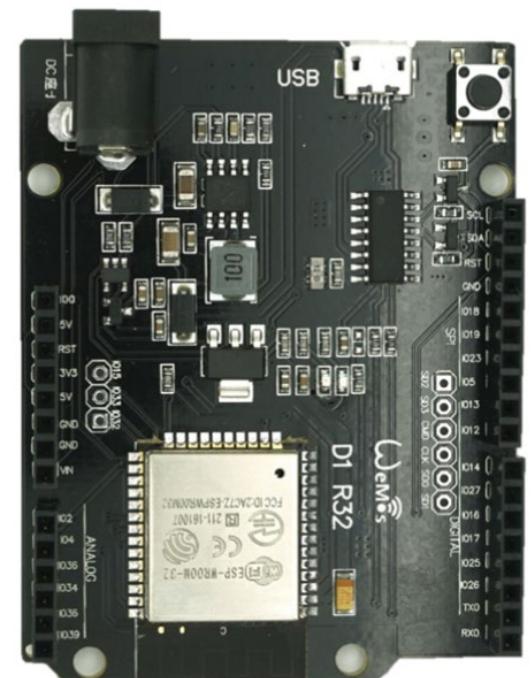

Wemos D1 R32 (based on ESP32)

# How to relate electronics to the physical world?

1. Measuring the appropriate variables (**SENSORS**)
2. Responding to those values (**Actuators**)


Microcontroller (*Arduino board or similar*) + Programming



# Garden



# IoT Garden

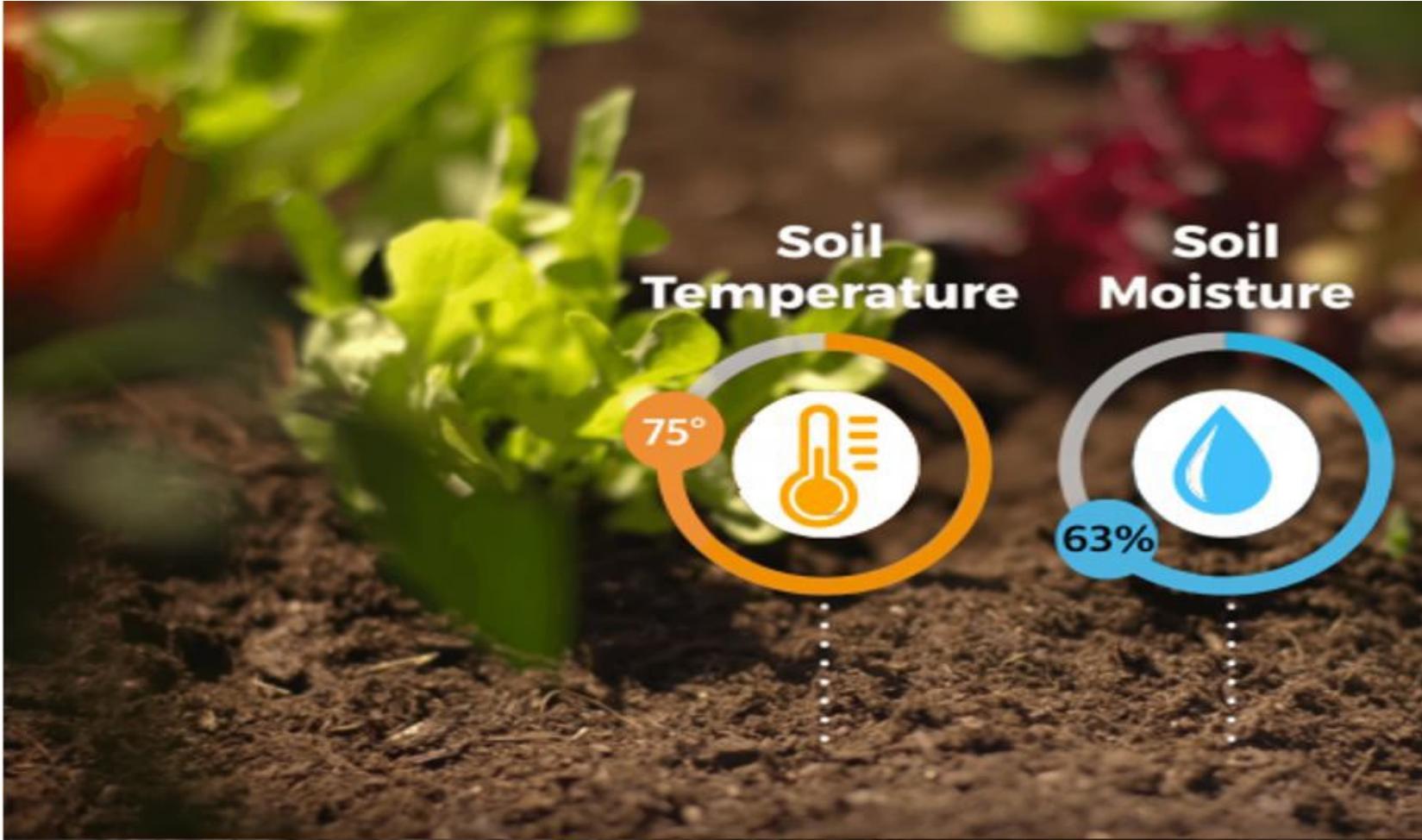



# An example about the use of electronics within Sensors and Actuators

## The LDR

# Sensor & Actuators


Temperature & Humidity sensor

Joystick



Buzzer

Motion detector

LDR

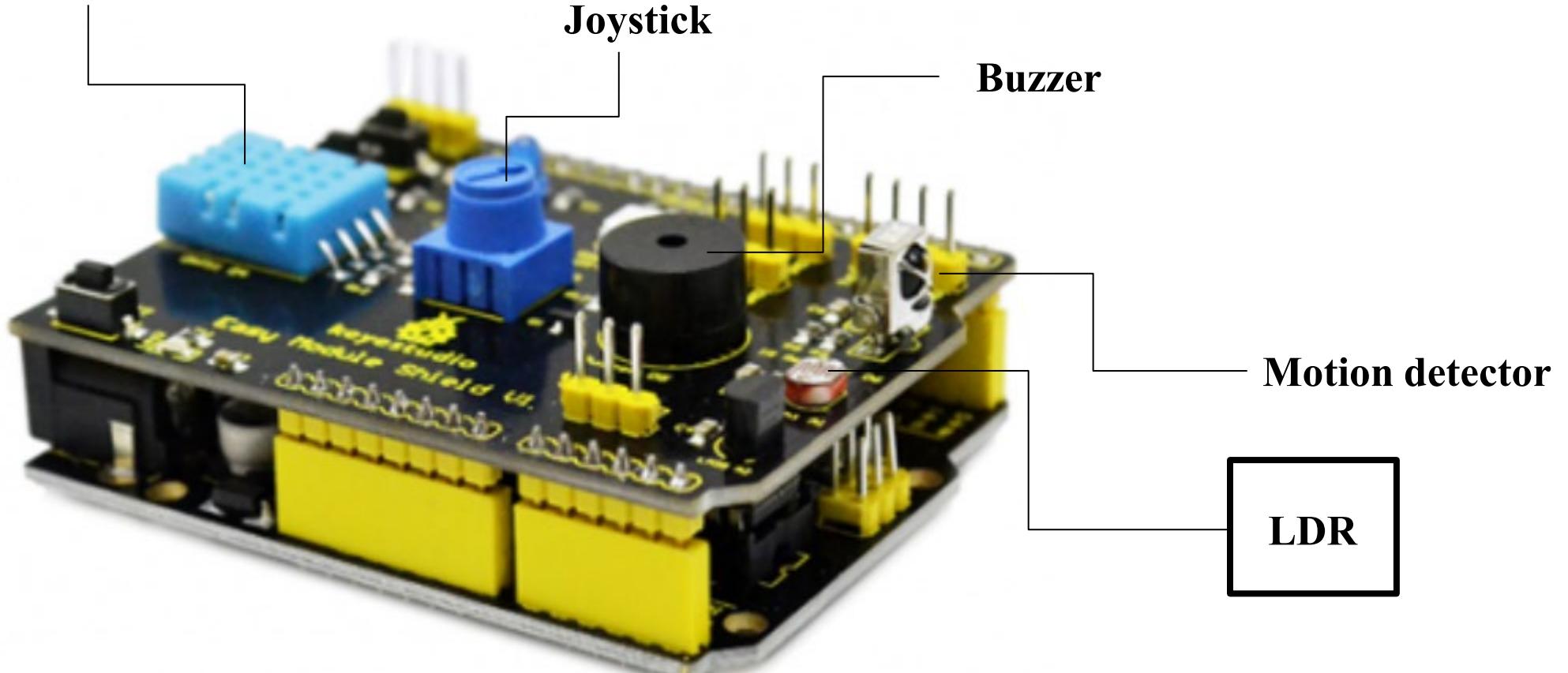

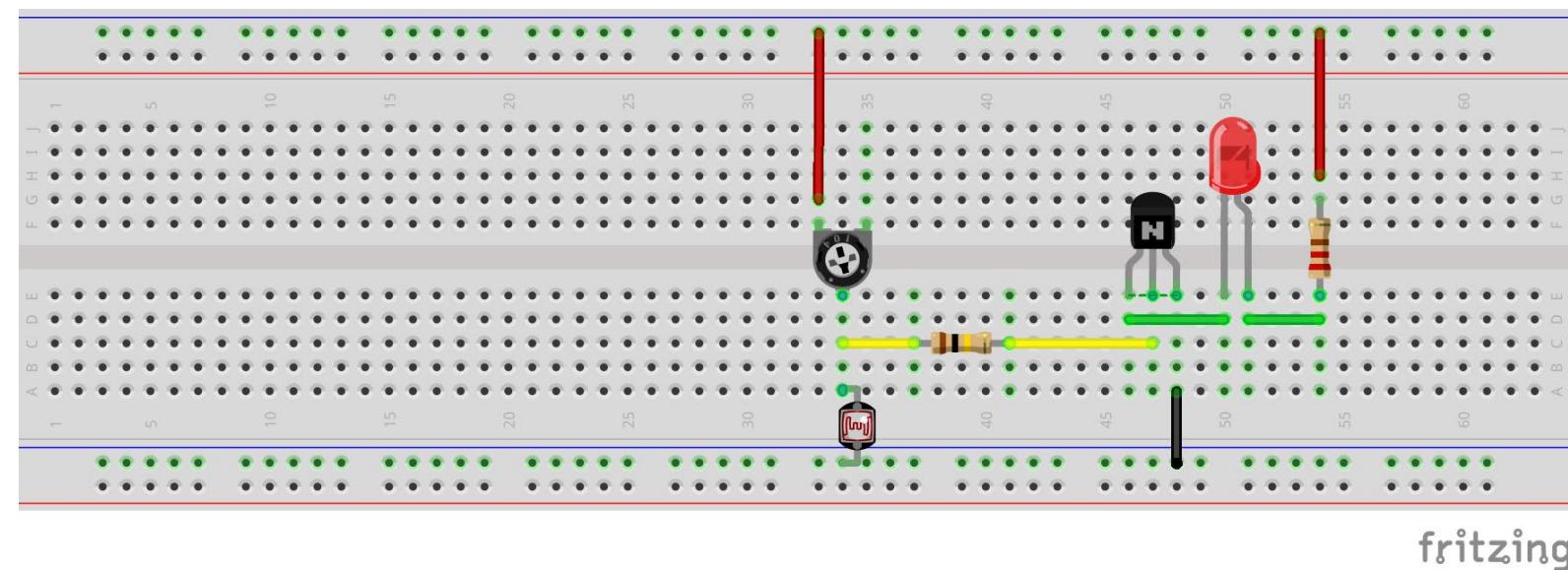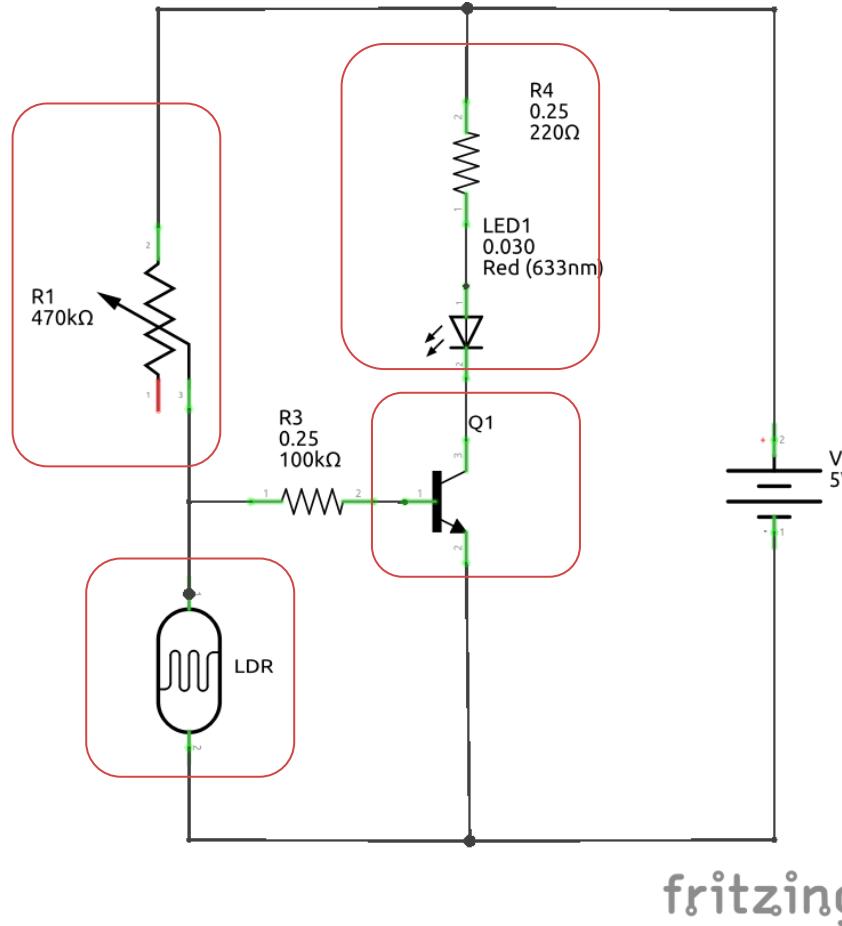1a. To design a circuit that turns on an LED when it becomes dark (BJT)



# Light Dependent Resistor (LDR)

- ✓ Resistance increases with decreasing light levels.
- ✓ A device with sensitivity in the visible light region, such as the NSL-19M51
  - In dark conditions, the resistance is high (up to a few  $M\Omega$ )
  - The resistance falls to less than  $1k\Omega$  in high light levels.





# Bipolar Junction Transistor (BJT)


If the base-emitter junction is forward-biased

$$I_B > 0 \text{ and } I_C > 0$$
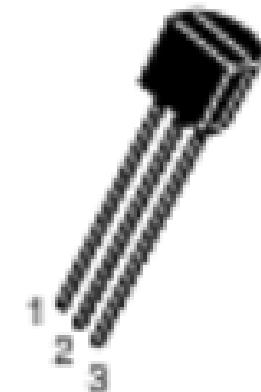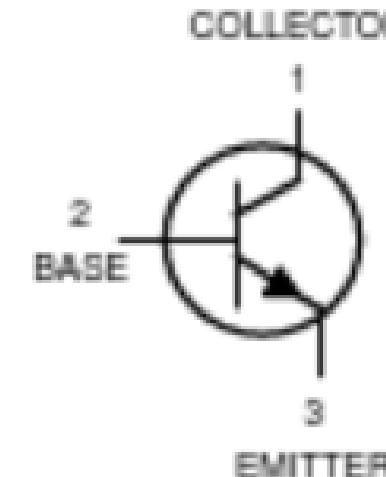
$$\text{In the active region } I_C = \beta * I_B$$


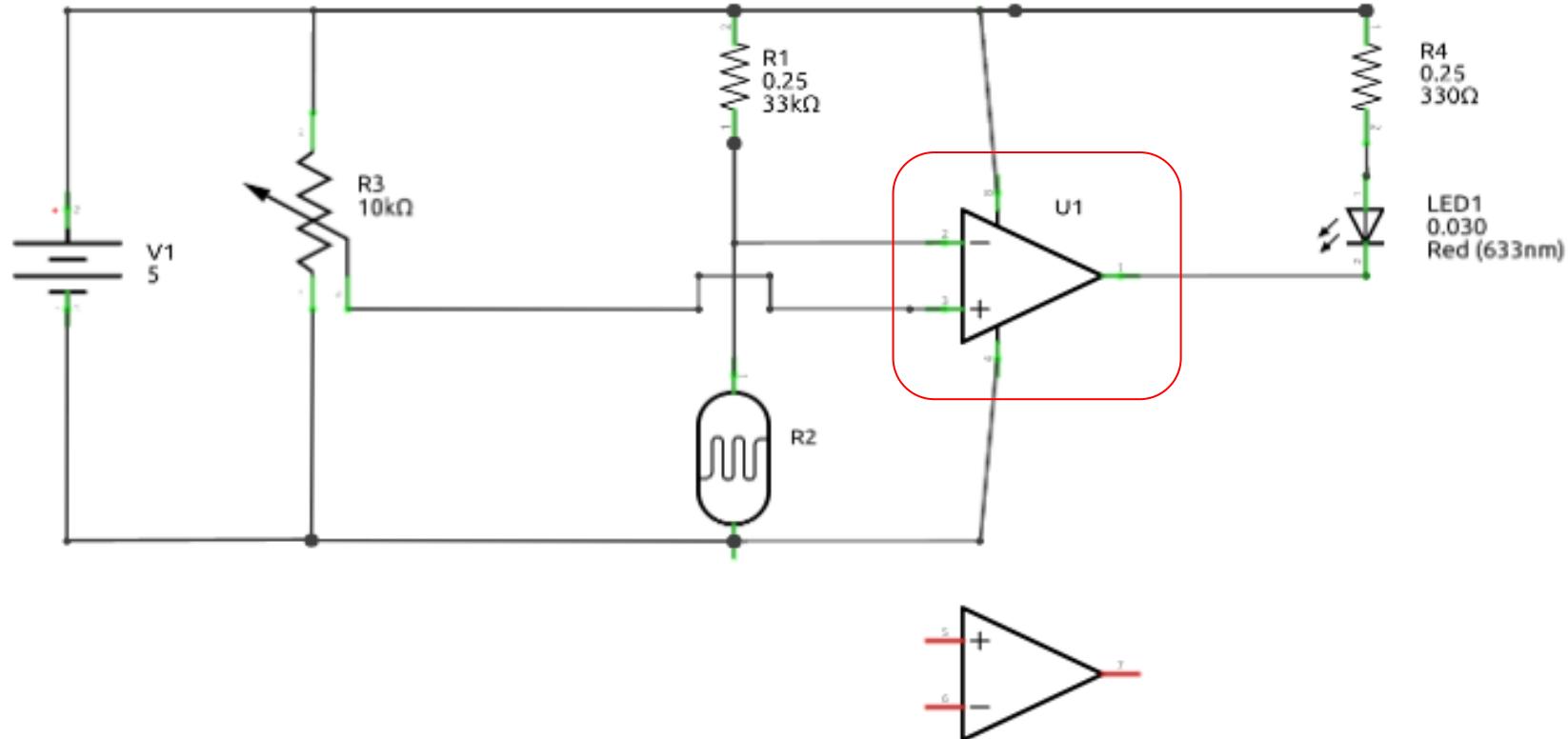
# 1b. To design a circuit that turns on an LED when it becomes dark (comparator)




fritzing

# Comparator

- ✓ The LM393 IC consists of two independent voltage comparators, each including two inputs ( $\text{IN}^+$ ,  $\text{IN}^-$ ) and one output (OUT).

✓ If  $V_{\text{IN}^+} > V_{\text{IN}^-}$  --->  $V_{\text{OUT}} = V_{\text{CC}}$

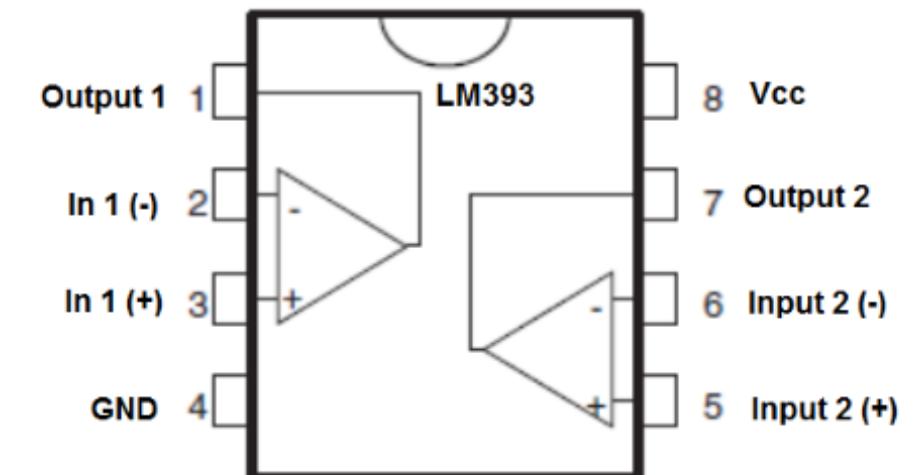✓ If  $V_{\text{IN}^+} < V_{\text{IN}^-}$  --->  $V_{\text{OUT}} = 0$




## 1b. Comparator

- ✓ The  $33k\Omega$  resistor and the LDR make up a **voltage divider**.
- ✓ Again, depending on the light level conditions, we first have **to set the reference voltage ( $V_+$ )** through the  $10K$  potentiometer in such a way that:

$$V_+ > V_- \quad (V_{OUT} = V_{cc})$$

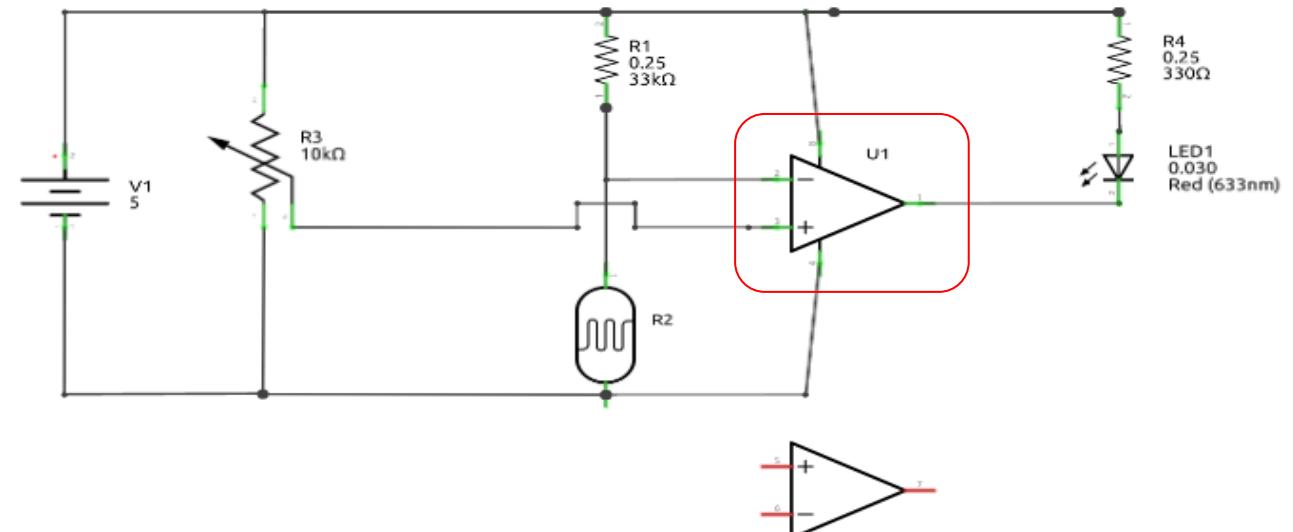**$V_+ < V_- \quad (V_{OUT} = 0 \rightarrow \text{LED ON})$**





THANK  
YOU